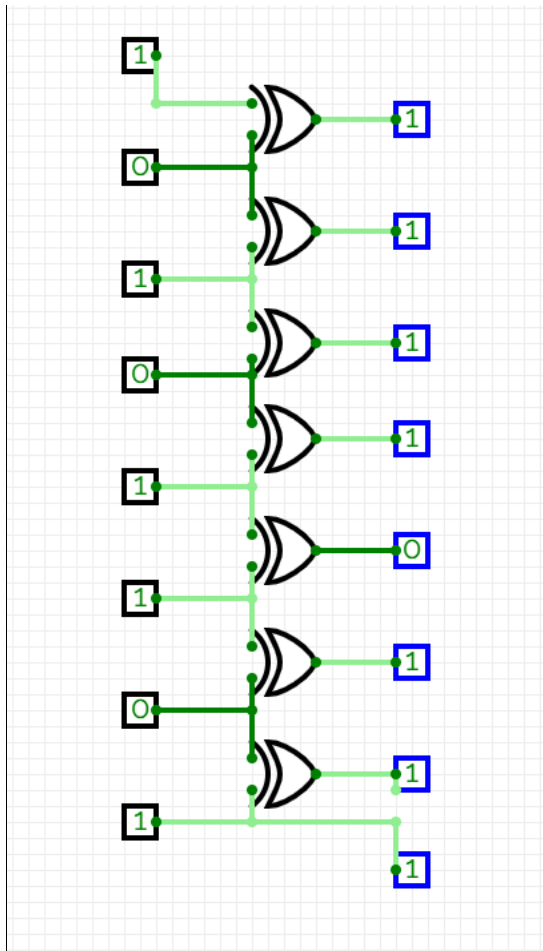


Habib University
Digital Logic and Design
EE/CE-172/222
Assignment 2 Fall 2025 Solution Manual

Question 1:

(a)



(b)

Binary counting can cause many bits to change simultaneously. Gray encoding guarantees that consecutive values differ in only one bit. During transitions, multiple simultaneous changes can cause errors or unstable signals. If Faaz's steps weren't converted to Gray code, these errors could be misread as wrong steps and Faaz may fall before creating the longest assignment.

Question: 02(a)

2pts

$$\rightarrow (x+y+z) + (x'+y'+z) + (w+x+y+z) + (w'+x'+y+z)$$

$$\rightarrow xy'z + xyz' + w'x'y'z + wxy'z'$$

x	y	z	w	$x+y+z'$	$x'+y'+z$	$w+x+y+z'$	$w'+x'+y+z$	F	$x'y'z$	xyz'	$x'y'zw'$	$xy'z'w$	F'
0	0	0	0	1	1	1	1	1	0	0	0	0	0
0	0	0	1	1	1	1	1	1	0	0	0	0	0
0	0	1	0	0	1	0	1	0	1	0	1	0	1
0	0	1	1	0	1	1	1	0	1	0	1	0	1
0	1	0	0	1	1	1	1	1	0	0	0	0	0
0	1	0	1	1	1	1	1	1	0	0	0	0	0
0	1	1	0	1	1	1	1	1	0	0	0	0	0
0	1	1	1	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	0	0	0	0	0
1	0	0	1	1	1	1	0	0	0	0	0	1	1
1	0	1	0	1	1	1	1	1	0	0	0	0	0
1	0	1	1	1	1	1	1	1	0	0	0	0	0
1	1	0	0	1	0	1	1	0	0	1	0	0	1

1	1	0	1	1	0	1	1	0	0	1	0	0	0	1
1	1	1	0	1	1	1	1	1	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	0	0	0	0	0	0

(b)

$$(a+b')(c+d')(a'+c)(b+d)(a'+b'+c+d')$$

2pts

$$(ab'+ac'+ad'+a'b'+b'+b'c'+b'd')(c+d')(a'b+a'd+bc+cd)$$

$$(b'[a+1+c'+d'] + ac'+ad'+a'b')(c+d')(a'b+a'd+bc+cd)$$

$$(b'+ac'+ad'+a'b')(a'bc+a'cd+bc+cd+a'bd'+bcd')$$

$$(b'+ac'+ad')(bc(a'+1+d') + cd(a'+1) + a'bd')$$

$$(b'+ac'+ad')(bc+cd+a'bd')$$

$$\boxed{b'cd + abcd'}$$

7 literal 2 terms

(c)

4pts

$$A \rightarrow 110101110011$$

$$B \rightarrow 101111001010$$

$$A \otimes B \rightarrow 011010111001$$

$$A \vee B \rightarrow 111111110110$$

$$A' \rightarrow 001010001100$$

Question: Q3 (a) 2pts

$$F_1 = ac + ad + b'c + b'd$$

$$F_1(\text{min}) = abcd + ab'cd + abcd' + ab'cd' + ab'c'd + abc'd + a'b'cd + a'b'cd' + a'b'c'd$$

$$\text{So, } F_1 = \sum(1, 2, 3, 9, 10, 11, 13, 14, 15)$$

$$F_2 = (ab' + cd)(a' + d)$$

$$F_2 = ab'd + a'cd + cd$$

$$F_2(\text{min}) = \overset{1011}{ab'cd} + \overset{1001}{ab'c'd} + \overset{0111}{a'bcd} + \overset{0011}{a'b'cd} + \overset{1111}{abcd}$$

$$F_2 = \sum(3, 7, 9, 11, 15)$$

$$\text{Let's compute } E = F_1 + F_2 = ac + ad + b'c + b'd + ab'd + a'cd + cd$$

$$E = ac + ad + b'c + b'd + cd$$

$$E(\text{min}) = abcd + ab'cd + abc'd + ab'c'd + abcd' + ab'cd' + a'bcd + a'b'cd + a'b'cd' + a'b'c'd$$

$$E(\text{min}) = \sum(1, 2, 3, 7, 9, 10, 11, 13, 14, 15)$$

Hence proved that E contains sum of minterms of F_1 and F_2

(b) 2pts

$$\text{Let's compute } G = F_1 \cdot F_2 =$$

$$G = (ac + ad + b'c + b'd) \cdot (ab'd + a'cd + cd)$$

$$G = \{ ab'cd + acd + ab'd + acd + ab'cd + a'b'cd + b'cd + b'cd + a'b'cd + b'cd \}$$

$$G = acd + \cancel{acd} + b'cd + a'b'cd + ab'd$$

$$G(\text{min}) = \overset{1111}{abcd} + \overset{1011}{ab'cd} + \overset{0011}{a'b'cd} + \overset{1001}{ab'cd}$$

$$G = \sum(3, 9, 11, 15) \text{ which are the common minterms of } F_1 \text{ and } F_2$$

Proved

a	b	c	d	F1	F2	E=cd+b'd+ac+ad+b'c	G=F1·F2
0	0	0	0	0	0	0	0
0	0	0	1	1	0	1	0
0	0	1	0	1	0	1	0
0	0	1	1	1	1	1	1
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	1	1	0
1	0	0	0	0	0	0	0
1	0	0	1	1	1	1	1
1	0	1	0	1	0	1	0
1	0	1	1	1	1	1	1
1	1	0	0	0	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	0	1	0
1	1	1	1	1	1	1	1

Question: 04 (a) 2pts


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

(b) 2pts

Minterms: $Z = A'BC + AB'C + ABC'$, $Z = \Sigma(3, 5, 6)$

Maxterms: $Z = (A+B+C)(A+B+C')(A+B'+C)(A'+B+C)(A'+B'+C')$

(c) 2pts

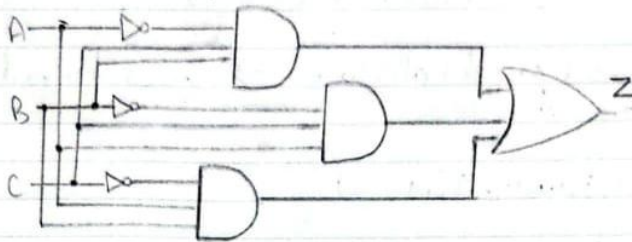

Question: 05 3pts

$$\overline{F} = [(ab+cd)' + (a'b'cd')' + (a+b'+c')' + (ab'+cd)' + (b+c+d')']$$

Considering all terms individually:

$$T_1 = (ab)'(cd)' = (a'+b')(c'+d) = a'c' + a'd + b'c' + b'd$$

$$T_2 = (a'b'c)d' = (a+b+c')d' = ad' + bd' + c'd'$$

$$T_3 = a'bc$$

$$T_4 = (ab')'(cd)' = (a'+b)(c'+d') = a'c' + a'd' + bc' + bd'$$

$$T_5 = b'c'd$$

Combining all four terms:

$$F' = a'c' + a'd + b'c' + b'd + ad' + bd' + c'd' + a'c' + a'd' + bc' + bd' + a'bc + b'c'd$$

$$F' = a'c' + a'(d+d') + b'c'(1+d) + b'd + ad' + c'd' + bc' + a'bc + bd'$$

$$F' = a'c' + a' + b'c' + b'd + ad' + c'd' + bc' + a'bc + bd'$$

$$F' = a' + c'(b'+b) + b'd + ad' + c'd' + a'bc$$

$$F' = a' + c' + b'd + ad' + c'd' + a'bc$$

$$F' = a' + c' + b'd + ad'$$

$$F' = (a'+a)(a'+d') + c' + b'd \quad \because x+yz = (x+y)(x+z)$$

$$F' = a' + d' + c' + b'd$$

$$F' = a' + c' + (d' + b')(d' + d)$$

$$F' = a' + b' + c' + d'$$

Question: 06

(a)

Product of Sum (PoS Form)

(b)

$$(A'+B)(C'D)^2(B'+C+D)$$

$$(A'+B)(B'C'D + 0 + C'D)$$

$$\rightarrow (A'+B)(C'D)$$


$$\rightarrow A'C'D + B'C'D$$

Question 7

(a) 2pts

w	x	y	z	$xy'z$	$x'y'z$	$w'xy$	$wx'y$	wxy	F
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	1
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0
0	1	0	1	1	0	0	0	0	1
0	1	1	0	0	0	1	0	0	1
0	1	1	1	0	0	1	0	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	1
1	0	1	0	0	0	0	1	0	1
1	0	1	1	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	0
1	1	0	1	1	0	0	0	0	1
1	1	1	0	0	0	0	0	1	1
1	1	1	1	0	0	0	0	1	1

(b) 2pts

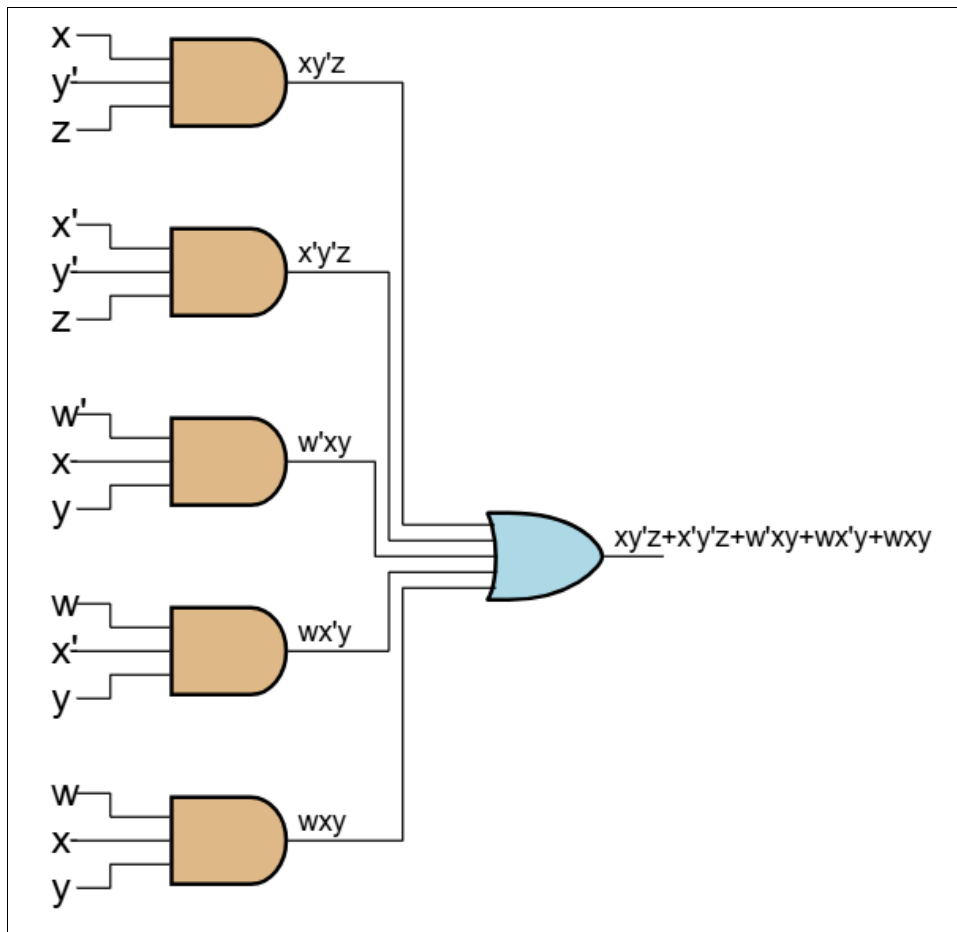

Question: 07

(c) 2pts


$$y'z(x+x') + xy(w'+w) + wx'y$$

$$y'z + xy + wx'y$$


$$y'z + y(x+wx') = y'z + y(x+w)$$

$$\boxed{y'z + yx + yw}$$


(d) 2pts

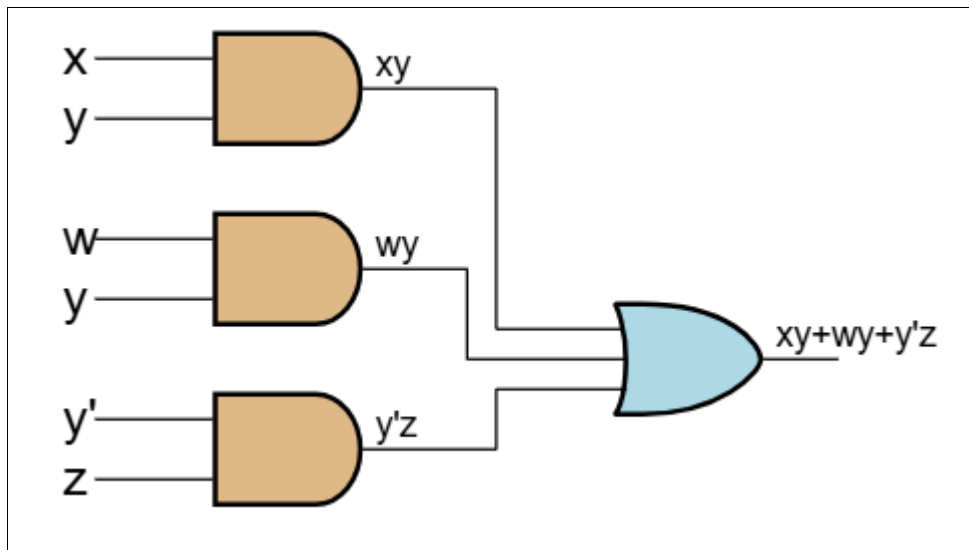

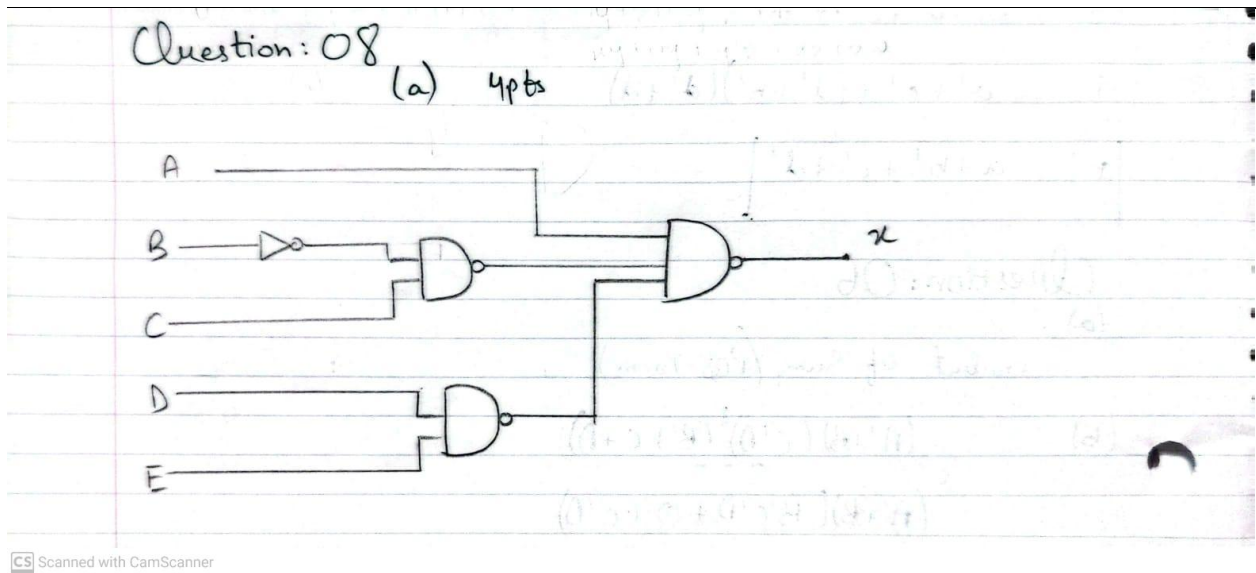The circuit uses 4 gates, compared to 6 gates from the original expressions circuit



(b) 2pts

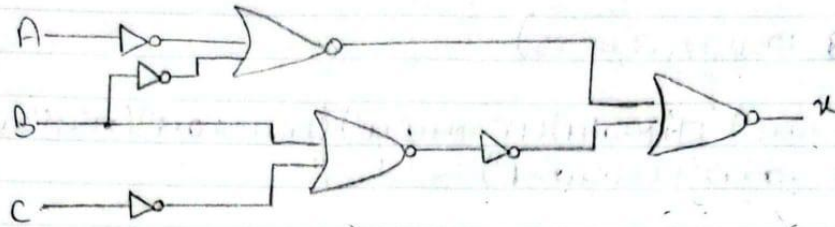

Question: 09

(a) 3pts

$$= (AB)'(C'D)'$$

$$\Rightarrow (A'+B')(C+D)$$

(b) 3pts

$$= (W'+X)(Y'XZ'+WZY)$$

$$= W'XY'Z' + XY'Z' + WZXY$$

$$= XY'Z' + WXYZ$$

(c) 3pts

$$= (P'+Q)(RS'PQ + RS')$$

$$= P'S'R + RS'PQ + RS'Q$$

$$= P'RS' + RS'Q$$

(d) 3pts

lets first find the minterms

$$F' = \overset{7}{M'NOP} + \overset{5}{M'NO'P} + \overset{6}{M'N'OP} + \overset{4}{M'N'O'P} + \overset{9}{MN'O'P} + \overset{1}{M'N'O'P} +$$

$$\overset{8}{MN'O'P'} + \overset{0}{M'N'O'P'} + \overset{2}{M'N'O'P'}$$

$$F' = \sum (0, 1, 2, 4, 5, 6, 7, 8, 9)$$

For minterms

$$F' = \prod (3, 10, 11, 12, 13, 14, 15)$$

$$F' = (M+N'+O+P')(M'+N+O+P)(M'+N+O'+P')(M'+N'+O+P)(M'+N'+O'+P')(M'+N'+O'+P')$$


(e) 4pts

$$F = (A'+B'+C)(A'B+A'C+BC)$$

$$= A'B + A'C + A'BC + A'B'C + A'BC + A'C + BC$$

$$= A'C(1+B+B') + A'B + BC$$

$$F = A'B + A'C + BC$$

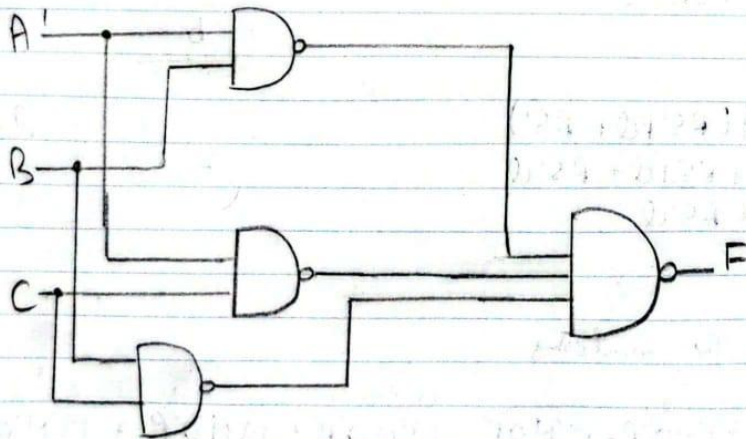

Question: 10

(a)

WX \ YZ	00	01	11	10
00	0			0
01		0		
11		0		
10	0	0	0	

3pts

$$F = (W+X+Z)(W'+X+Y)(W'+X+Z')(X'+Y+Z')(W'+Y+Z')$$

(b)

AB \ CD	00	01	11	10
00	1	X		1
01		X		1
11			1	1
10		X		1

3pts

$$F = A'B'C' + ABC + CD'$$

Question: 11

(a)

AB \ CD	00	01	11	10
00		1		
01	X	1		1
11	1	1		1
10			1	

5pts

$$X = A'C'D + BC' + BCD' + AB'CD$$


(b)

AB \ CD	00	01	11	10
00	0		0	
01	X	0	0	
11			0	
10		0	0	0


$$Y = (A+C+D)(A+B'+D')(C'+D')(A'+B+D')(A'+B+C')$$

(b) 5pts

X:

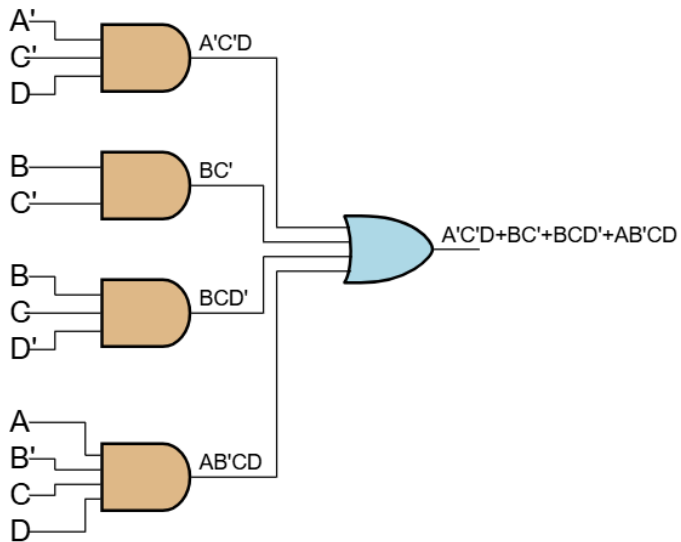

Y:

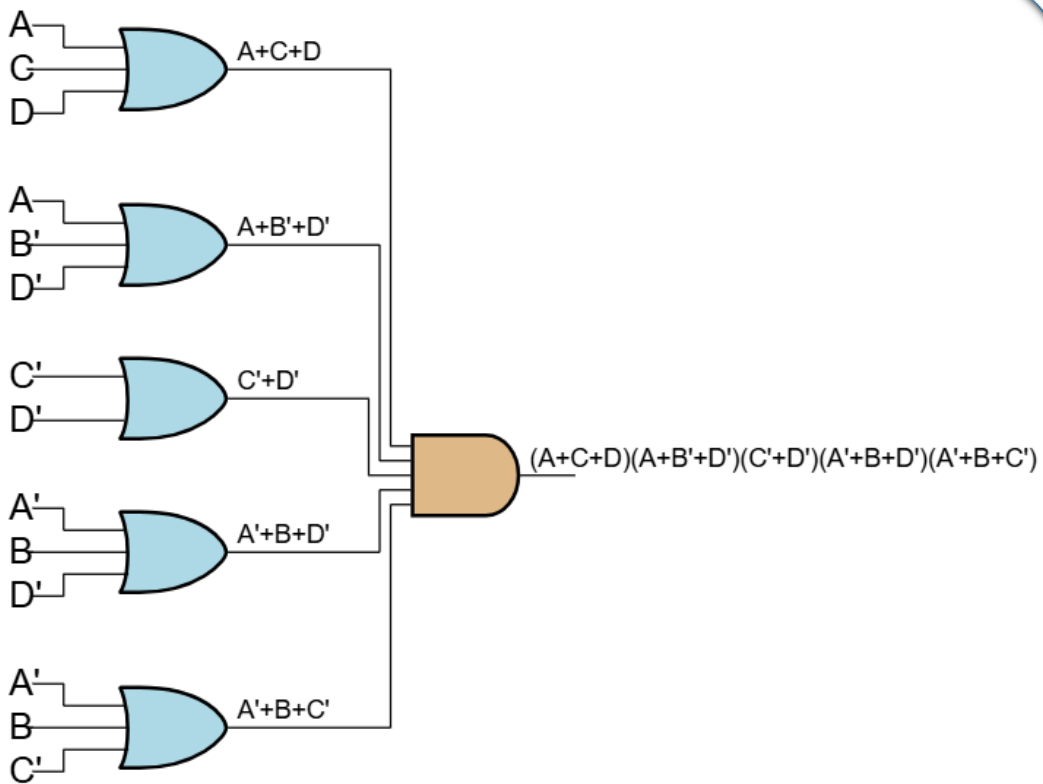

Question: 12
(a)

3pts

$$(W + Y + [(W + Y)Z]')(WY')$$

$$(W + Y + ((W + Y)' + Z'))(WY')$$

$$(W + Y + W'Y' + Z')(WY')$$

$$WY' + WY'Z = WY'$$

CS Scanned with CamScanner

$$WXYZ Y' F = W \cdot Y'$$

0 0 0 1 0

0 0 0 1 1 0

0 0 1 0 0 0

0 0 1 1 0 0

0 1 0 0 1 0

0 1 0 1 1 0

0 1 1 0 0 0

0 1 1 1 0 0

1 0 0 0 1 1

1 0 0 1 1 1

1 0 1 0 0 0

1 0 1 1 0 0

1 1 0 0 1 1

1 1 0 1 1 1

$$W X Y Z Y' F = W \cdot Y'$$

1 1 1 0 0 0

1 1 1 1 0 0

(C)

Karnaugh map

	$\overline{y}z$	$\overline{y}z$	$y\overline{z}$	$y\overline{z}$
$\overline{w}x$	0	0	0	0
$w\overline{x}$	0	0	0	0
wx	1	1	0	0
$\overline{w}x$	1	1	0	0

(D)


Only 1 gate will be used as compared to the 5 gates in the original logic

Question: 13 (a) 4pts

wx \ yz	00	01	11	10
00	1	1	1	1
01		1	1	1
11	1	1	1	1
10	1			

$$F = wY'z' + w'x' + wX + xY$$

(b)

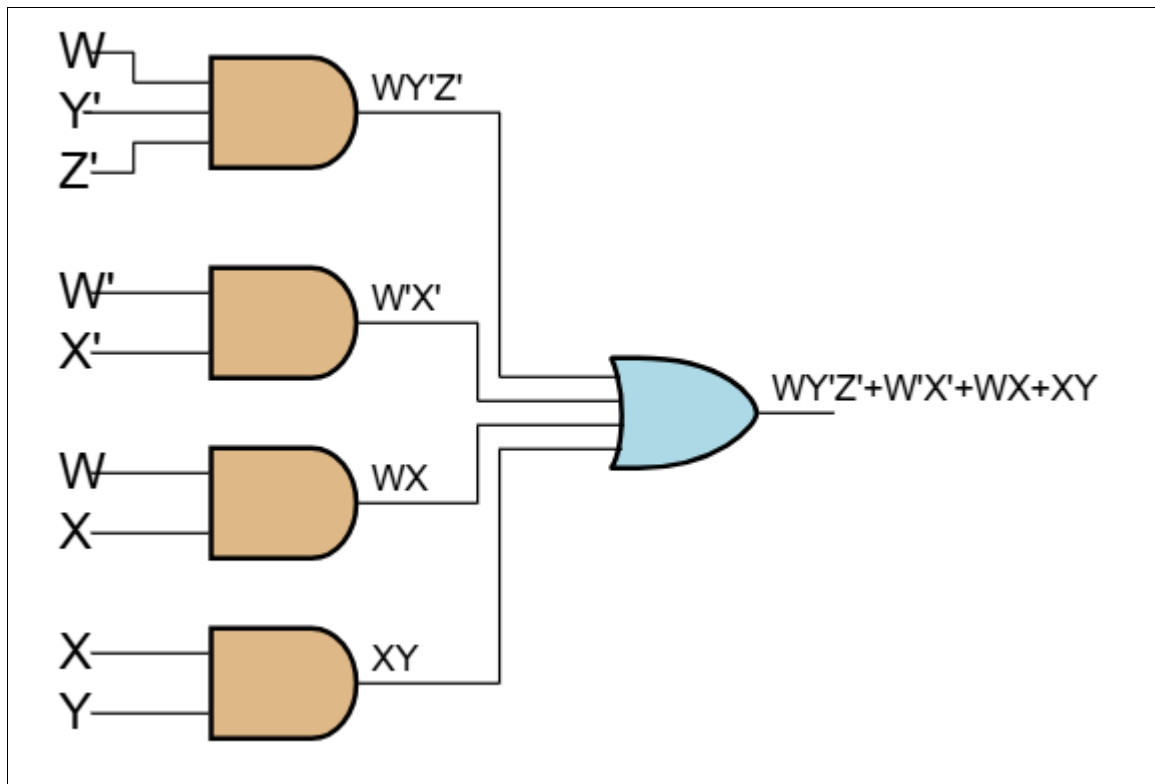

(c) — 3pts

There are 8 minterms in the original expression and each will have 4 literals. Whereas in the simplified form, there are 4 terms with 2 and 3 literals.

(d) 3pts

