

# Computer Architecture

(EE 371 / CE 321 / CS 330)


Dr. Farhan Khan  
Assistant Professor,  
Dhanani School of Science & Engineering,  
Habib University

# Outline: Unit 3

- Arithmetic for Computers: Review
- Digital Logic Design: Review
- Arithmetic Logic Unit (ALU)
- Single-Cycle Processor Implementation
 
# Integer Addition

$$\begin{array}{r}
 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000111_{\text{two}} - 7_{\text{ten}} \\
 +\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000110_{\text{two}} - 6_{\text{ten}} \\
 \hline
 -\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00001101_{\text{two}} - 13_{\text{ten}}
 \end{array}$$



# Integer Addition: Overflow

$$\begin{array}{r} 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000111_{\text{two}} - 7_{\text{ten}} \\ +\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000110_{\text{two}} - 6_{\text{ten}} \\ \hline -\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00001101_{\text{two}} - 13_{\text{ten}} \end{array}$$

Overflow occurs when the result from an operation cannot be represented with the available hardware, in this case a 64-bit word

- Adding +ve and -ve operands
  - Overflow is not possible
- Adding two +ve number
  - Overflow has occurred if the sign bit of the result is 1
- Adding two -ve numbers
  - Overflow has occurred if the sign bit of the result is 0

# Integer Subtraction

- Subtraction through Addition
  - Add first operand and negation of the second operand
  - Example:  $7 - 6 = 7 + (-6)$

$$\begin{array}{r} 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000111_{\text{two}} - 7_{\text{ten}} \\ +\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111010_{\text{two}} - -6_{\text{ten}} \\ \hline =\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000001_{\text{two}} - 1_{\text{ten}} \end{array}$$


# Integer Subtraction: Overflow

$$\begin{array}{r} 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000111_{\text{two}} - 7_{\text{ten}} \\ +\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111111\ 11111010_{\text{two}} - -6_{\text{ten}} \\ \hline =\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000000\ 00000001_{\text{two}} - 1_{\text{ten}} \end{array}$$

Overflow occurs when the result from an operation cannot be represented with the available hardware, in this case a 64-bit word


- Subtracting two +ve or two -ve operands
  - Overflow is not possible
- Subtracting +ve from -ve operand
  - Overflow has occurred if the sign bit of the result is 0
- Subtracting -ve from +ve operands
  - Overflow has occurred if the sign bit of the result is 1

# Review of Logic Design

 


# Review of Logic Design

- 2 Types of Logic Systems

 

 The output of a combinational logic system depends only on the current input.



The output of a sequential logic system can depend both on the inputs and internal memory.



# Review of Logic Design


- Truth Table

- Because a combinational logic block contains no memory, it can be completely specified by defining the values of the outputs for each possible set of input values.
- Such a description is normally given as a truth table.

| Inputs |   |   | Outputs |   |   |
|--------|---|---|---------|---|---|
| A      | B | C | D       | E | F |
| 0      | 0 | 0 | 0       | 0 | 0 |
| 0      | 0 | 1 | 1       | 0 | 0 |
| 0      | 1 | 0 | 1       | 0 | 0 |
| 0      | 1 | 1 | 1       | 1 | 0 |
| 1      | 0 | 0 | 1       | 0 | 0 |
| 1      | 0 | 1 | 1       | 1 | 0 |
| 1      | 1 | 0 | 1       | 1 | 0 |
| 1      | 1 | 1 | 1       | 0 | 1 |

 
# Review of Logic Design

- Logic Gates
  - Logic blocks/systems are built from Logic Gates that implement basic logic functions


 
# Review of Logic Design

- Decoder
  - The decoder has an n-bit input and  $2^n$  outputs, where only one output is asserted for each input combination




a. A 3-bit decoder

| Inputs |    |    | Outputs |      |      |      |      |      |      |      |
|--------|----|----|---------|------|------|------|------|------|------|------|
| 12     | 11 | 10 | Out7    | Out6 | Out5 | Out4 | Out3 | Out2 | Out1 | Out0 |
| 0      | 0  | 0  | 0       | 0    | 0    | 0    | 0    | 0    | 0    | 1    |
| 0      | 0  | 1  | 0       | 0    | 0    | 0    | 0    | 0    | 1    | 0    |
| 0      | 1  | 0  | 0       | 0    | 0    | 0    | 0    | 1    | 0    | 0    |
| 0      | 1  | 1  | 0       | 0    | 0    | 0    | 1    | 0    | 0    | 0    |
| 1      | 0  | 0  | 0       | 0    | 0    | 1    | 0    | 0    | 0    | 0    |
| 1      | 0  | 1  | 0       | 0    | 1    | 0    | 0    | 0    | 0    | 0    |
| 1      | 1  | 0  | 0       | 1    | 0    | 0    | 0    | 0    | 0    | 0    |
| 1      | 1  | 1  | 1       | 0    | 0    | 0    | 0    | 0    | 0    | 0    |

b. The truth table for a 3-bit decoder
 
# Review of Logic Design


- Multiplexor (Selector)
  - Consider the two-input multiplexor.
  - This multiplexor has three inputs: two data values and a selector (or control) value.
  - The selector value determines which of the inputs becomes the output.


 
# Review of Logic Design

- Multiplexor (Selector)


- Consider the two-input multiplexor.
- This multiplexor has three inputs: two data values and a selector (or control) value.
- The selector value determines which of the inputs becomes the output.



- Multiplexors can be created with an arbitrary number of data inputs.
 
# Arithmetic Logic Unit (ALU)


- The arithmetic logic unit (ALU) is the brain of the computer, the device that performs the arithmetic operations like addition and subtraction or logical operations like AND and OR.



# Arithmetic Logic Unit (ALU)

- The arithmetic logic unit (ALU) is the brain of the computer, the device that performs the arithmetic operations like addition and subtraction or logical operations like AND and OR.
- Let's focus on 1-bit ALU and progressively build an ALU with more functionality


# Arithmetic Logic Unit (ALU)

 

The 1-bit Logical Unit for AND and OR.




# 1-bit Adder

 


| Inputs |   |         | Outputs  |     | Comments                      |
|--------|---|---------|----------|-----|-------------------------------|
| a      | b | CarryIn | CarryOut | Sum |                               |
| 0      | 0 | 0       | 0        | 0   | $0 + 0 + 0 = 00_{\text{two}}$ |
| 0      | 0 | 1       | 0        | 1   | $0 + 0 + 1 = 01_{\text{two}}$ |
| 0      | 1 | 0       | 0        | 1   | $0 + 1 + 0 = 01_{\text{two}}$ |
| 0      | 1 | 1       | 1        | 0   | $0 + 1 + 1 = 10_{\text{two}}$ |
| 1      | 0 | 0       | 0        | 1   | $1 + 0 + 0 = 01_{\text{two}}$ |
| 1      | 0 | 1       | 1        | 0   | $1 + 0 + 1 = 10_{\text{two}}$ |
| 1      | 1 | 0       | 1        | 0   | $1 + 1 + 0 = 10_{\text{two}}$ |
| 1      | 1 | 1       | 1        | 1   | $1 + 1 + 1 = 11_{\text{two}}$ |

# Arithmetic Logic Unit (ALU)

 


The 1-bit Logical Unit for AND and OR.

 


The 1-bit ALU that performs AND, OR, and addition.

# Arithmetic Logic Unit (ALU)

 


A 64-bit ALU constructed from 64 1-bit ALUs

# Arithmetic Logic Unit (ALU)

 

 
The 1-bit ALU that performs AND, OR, and addition.




Support for subtraction (through addition).

- By selecting b (Binvert = 1) and setting CarryIn to 1 in the least significant bit of the ALU, we get two's complement subtraction of b from a instead of addition of b to a.

# Arithmetic Logic Unit (ALU)

 

 The 1-bit ALU that performs AND, OR, addition, and subtraction (through addition).





Support for NOR operation (through AND).

- DeMorgan's Theorem .

$$\overline{(a + b)} = \bar{a} \cdot \bar{b}$$

# Arithmetic Logic Unit (ALU)

  

The 1-bit ALU that performs AND, OR, addition, subtraction (through addition) and NOR operation.

Support for slt operation.



slt rd, rs1, rs2

rd = 1 if rs1 < rs2

rd = 0 otherwise

- Consequently, slt will set all but the least significant bit to 0, with the least significant bit set according to the comparison.

# Arithmetic Logic Unit (ALU)

  


The 1-bit ALU that performs AND, OR, addition, subtraction (through addition) and NOR operation.

Support for slt operation.

- For the ALU to perform slt, we first need to expand the three-input multiplexor to add an input for the slt result. We call that new input Less and use it only for

# Arithmetic Logic Unit (ALU)

 




## Support for slt operation.

- We must connect 0 to the Less input for the upper 63 bits of the ALU, since those bits are always set to 0.
- How to set the least significant bit?
  - We want the least significant bit of slt operation to be a 1 if  $a < b$
  - That is, we want the least significant bit of slt operation to be a 1 if  $a - b$  is negative and a 0 if  $a - b$  is positive
  - This desired result corresponds exactly to the sign bit values after performing  $a - b$ : 1 means negative and 0 means positive
  - So, we need only connect the sign bit (adder output of the most significant bit) to the Less input of least significant bit to get slt.
  - This needs a modified 1-bit ALU at the most significant bit

A 64-bit ALU constructed from 64 1-bit ALUs (Notice the ALU for Most Significant Bit)



# Arithmetic Logic Unit (ALU)

   


Most significant bit

The 1-bit ALU that performs AND, OR, addition, subtraction (through addition) and NOR operation.

## Support for slt operation.

- We need to connect the sign bit (adder output of the most significant bit) to the Less input of least significant bit to get slt.
- This needs a modified 1-bit ALU at the most significant bit (addition of the Set output)

# Arithmetic Logic Unit (ALU)

 


## Support for slt operation.

- We must connect 0 to the Less input for the upper 63 bits of the ALU, since those bits are always set to 0.
- How to set the least significant bit?
  - We want the least significant bit of slt operation to be a 1 if  $a < b$
  - That is, we want the least significant bit of slt operation to be a 1 if  $a - b$  is negative and a 0 if  $a - b$  is positive
  - This desired result corresponds exactly to the sign bit values after performing  $a - b$ : 1 means negative and 0 means positive
  - So, we need only connect the sign bit (adder output of the most significant bit) to the Less input of least significant bit to get slt.
  - This needs a modified 1-bit ALU at the most significant bit

A 64-bit ALU constructed from 64 1-bit ALUs (Notice the ALU for Most Significant Bit)

# Arithmetic Logic Unit (ALU)

 


## Support for beq operation.

- beq operation branches if two registers are equal.
- The easiest way to test equality with the ALU is to subtract b from a and then test to see if the result is 0.
- To test if the result is 0, the simplest way is to OR all the outputs together and then send that signal through an inverter

$$\text{Zero} = \overline{(\text{Result63} + \text{Result62} + \dots + \text{Result2} + \text{Result1} + \text{Result0})}$$

# Arithmetic Logic Unit (ALU)

 


## Simplifying Control

- Notice that every time we want the ALU to subtract, we set both CarryIn and Binvert to 1.
- For adds or logical operations, we want both control lines to be 0.
- We can therefore simplify control of the ALU by combining the CarryIn and Binvert to a single control line called Bnegate.

# Arithmetic Logic Unit (ALU)
 
## Simplifying Control

- Notice that every time we want the ALU to subtract, we set both CarryIn and Binvert to 1.
- For adds or logical operations, we want both control lines to be 0.
- We can therefore simplify control of the ALU by combining the CarryIn and Binvert to a single control line called Bnegate.




# Arithmetic Logic Unit (ALU)


## ALU Control

- We can think of the combination of the 1-bit Ainvert line, the 1-bit Bnegate line, and the 2-bit Operation lines as **4-bit control lines for the ALU**, telling it to perform add, subtract, AND, OR, NOR, or set less than.

| ALU control lines | Function      |
|-------------------|---------------|
| 0000              | AND           |
| 0001              | OR            |
| 0010              | add           |
| 0110              | subtract      |
| 0111              | set less than |
| 1100              | NOR           |

 

# Arithmetic Logic Unit (ALU)

 

Symbol for a Complete ALU